

# **ELECTRONIC CIRCUIT ANALYSIS (15A04401)**

## **Multiple Choice Questions**

### **UNIT-1**

1. The gain of an amplifier with Negative feedback is given by  $A_f =$  \_\_\_\_\_.  
a)  $A/(1+A\beta)$                       b)  $A/(1-A\beta)$     c)  $A+1/(A\beta)$                       d)  $A-1/(A\beta)$
2. The disadvantage of negative feedback is that gain \_\_\_\_\_.  
a) high gain                      b) high distortion                      c) less gain                      d) less distortion
3. With series feedback, input resistance of an amplifier will \_\_\_\_\_.  
a) decrease                      b) increase                      c) remains constant                      d) increase or decrease
4. If negative feedback is used in amplifiers then Noise will \_\_\_\_\_.  
a) decrease                      b) increase                      c) remains constant                      d) increase or decrease
5. If negative feedback is used in amplifiers then Bandwidth will \_\_\_\_\_.  
a) decrease                      b) increase                      c) remains constant                      d) increase or decrease
6. If negative feedback is used in amplifiers then lower cut-off frequency will \_\_\_\_\_.  
a) decrease                      b) increase                      c) remains constant                      d) increase or decrease
7. If negative feedback is used in amplifiers then higher cut-off frequency will \_\_\_\_\_.  
a) decrease                      b) increase                      c) remains constant                      d) increase or decrease
8. If negative feedback is used in amplifiers then gain will \_\_\_\_\_.  
a) be unity    b) increase                      c) remains constant                      d) decrease
9. If negative feedback is used in amplifiers then distortion will \_\_\_\_\_.  
a) remains constant    b) increase                      c) decrease                      d) be zero
10. With shunt feedback, input resistance of an amplifier will \_\_\_\_\_.  
a) decrease                      b) increase                      c) remains constant                      d) zero
11. Voltage series feedback amplifier is also called as \_\_\_\_\_ amplifier.  
a) Transresistance    b) Transconductance    c) current    d) voltage
12. Voltage shunt feedback amplifier is also called as \_\_\_\_\_.  
a) Transresistance    b) Transconductance    c) voltage    d) current
13. Current series feedback amplifier is also called as \_\_\_\_\_.  
a) Transresistance    b) Transconductance    c) voltage    d) current
14. Current shunt feedback amplifier is also called as \_\_\_\_\_.  
a) Transresistance    b) Transconductance    c) voltage    d) current
15. Oscillator is a circuit which converts \_\_\_\_\_ to \_\_\_\_\_.  
a) ac, dc                      b) ac, ac                      c) dc, ac                      d) dc, dc
16. Sinusoidal oscillators are also called as \_\_\_\_\_ oscillators.  
a) NonHarmonic                      b) Relaxation                      c) Harmonic    d) negative feedback
17. Non-Sinusoidal oscillators are also called as \_\_\_\_\_.

a) Harmonic                      b) Relaxation                      c) non-relaxation                      d) negative feedback

18. Classification of oscillators based on type of circuit are divided into \_\_\_\_\_ and \_\_\_\_\_.

a) LC oscillators                      b) RC oscillators                      c) both a, b                      d) -ve resistance oscillators

19. Examples of non-sinusoidal waveforms are \_\_\_\_\_.

a) square                      b) sawtooth                      c) triangular                      d) all

20. An oscillator uses \_\_\_\_\_ feedback.

a) positive                      b) zero                      c) negative                      d) both positive, negative

21. RF oscillators are also called as \_\_\_\_\_ oscillators.

a) High Frequency                      b) Very High Frequency                      c) Low Frequency                      d) Microwave Frequency

22. AF oscillator has \_\_\_\_\_ range of frequencies.

a) 30MHz-300MHz                      b) 20KHz-30MHz                      c) up to 20KHz                      d) above 3GHz

23. RF oscillator has \_\_\_\_\_ range of frequencies.

a) up to 20KHz                      b) 20KHz-30MHz                      c) 30MHz-300MHz                      d) above 3GHz

24. VHF oscillator has \_\_\_\_\_ range of frequencies.

a) up to 20KHz                      b) 20KHz-30MHz                      c) 30MHz-300MHz                      d) above 3GHz

25. UHF oscillator has \_\_\_\_\_ range of frequencies.

a) 300MHz -3GHz                      b) 20KHz-30MHz                      c) 30MHz-300MHz                      d) above 3GHz

26. MWF oscillator has \_\_\_\_\_ range of frequencies.

a) 300MHz -3GHz                      b) 20KHz-30MHz                      c) 30MHz-300MHz                      d) above 3GHz

27. Examples of LC oscillators are \_\_\_\_\_ circuits.

a) Hartley, Colpitts                      b) Weinbridge, Colpitts                      c) Hartley, RC phase shift                      d) Weinbridge, RC phase shift

28. Examples of RC oscillators are \_\_\_\_\_ circuits.

a) Hartley, Colpitts                      b) Weinbridge, RC phase shift                      c) Hartley, RC phase shift                      d) Weinbridge, Colpitts

29. \_\_\_\_\_ Oscillator exhibits piezoelectric effect.

a) Hartley, Colpitts                      b) Weinbridge, Colpitts                      c) Hartley, RC phase shift                      d) Crystal

30. Necessary conditions to be satisfied by any oscillator circuit are called as \_\_\_\_\_.

a) Halls criteria                      b) DeMorgans criteria                      c) Millers Criteria                      d) Barkhausen Criteria

31. Two conditions to be satisfied by any oscillator circuit are given by \_\_\_\_\_ and \_\_\_\_\_.

a)  $|A\beta|=0, \theta=1^0$                       b)  $|A\beta|=1, \theta=0^0$                       c)  $|A\beta|=1, \theta=90^0$                       d)  $|A\beta|=0, \theta=180^0$

32. Advantage of RC oscillator is \_\_\_\_\_.

a) less cost                      b) high B.W                      c) high gain                      d) used for VHF range

33. RC phase shift oscillator has \_\_\_\_\_ no. of identical RC sections.

a) 1                      b) 2                      c) 3                      d) 4

34. Each RC section in RC phase shift oscillator generates \_\_\_\_\_ degrees of phase shift.

a) 30                      b) 60                      c) 90                      d) 180

35. Advantage of LC oscillator is \_\_\_\_\_.

a) less cost                      b) high B.W                      c) high gain                      d) used for VHF range



14. Range of  $C_{b'e}$  is \_\_\_\_\_.

- a) 1pF                      b) 3pF                      c) 100pF                      d) 50pF

15. Formula of  $r_{bb'}$  is \_\_\_\_\_.

- a)  $h_{ie} + r_{be}$                       b)  $h_{ie} - r_{be}$                       c)  $h_{fe}/g_m$                       d)  $r_{be}/h_{re}$

16. Formula of  $r_{b'c}$  is \_\_\_\_\_.

- a)  $h_{ie} + r_{be}$                       b)  $h_{ie} - r_{be}$                       c)  $h_{fe}/g_m$                       d)  $r_{be}/h_{re}$

17. Formula of  $r_{b'e}$  is \_\_\_\_\_.

- a)  $h_{ie} + r_{be}$                       b)  $h_{ie} - r_{be}$                       c)  $h_{fe}/g_m$                       d)  $r_{be}/h_{re}$

18. Formula of  $g_m$  is \_\_\_\_\_.

- a)  $I_c/V_t$                       b)  $h_{ie} - r_{be}$                       c)  $h_{fe}/g_m$                       d)  $r_{be}/h_{re}$

19. Formula of  $V_T$  in terms of T in  $^{\circ}C$  is \_\_\_\_\_.

- a) T/1160                      b) T/10600                      c) T/1160                      d) T/11600

20. Formula of  $h_{ie}$  in terms of  $r_{bb'}$  is \_\_\_\_\_.

- a)  $r_{bb'} + r_{be}$                       b)  $r_{bb'} - r_{be}$                       c)  $r_{bb'}/r_{be}$                       d)  $r_{bb'} \cdot r_{be}$

21. Formula of Bandwidth is \_\_\_\_\_.

- a)  $f_1 - f_2$                       b)  $f_1 + f_2$                       c)  $f_2 - f_1$                       d)  $(f_2 + f_1)/2$

22.  $f_T$  is called as \_\_\_\_\_.

- a) gain bandwidth product      b) transmission frequency      c)  $\beta$  cut off frequency      d)  $\alpha$  cutoff frequency

23.  $f_{\beta}$  is called as \_\_\_\_\_.

- a) gain bandwidth product      b) transmission frequency      c)  $\beta$  cut off frequency      d)  $\alpha$  cutoff frequency

24.  $f_{\alpha}$  is called as \_\_\_\_\_.

- a) gain bandwidth product      b) transmission frequency      c)  $\beta$  cut off frequency      d)  $\alpha$  cutoff frequency

25.  $f_{\beta}$  is also indicated as \_\_\_\_\_.

- a)  $f_{hfb}$                       b)  $f_{hfe}$                       c)  $f_{hfc}$                       d)  $f_T$

26.  $f_{\alpha}$  is also indicated as \_\_\_\_\_.

- a)  $f_{hfb}$                       b)  $f_{hfe}$                       c)  $f_{hfc}$                       d)  $f_T$

27.  $f_T$  in terms of  $f_{\alpha}$  is given by \_\_\_\_\_.

- a)  $f_T = h_{fe} f_{\alpha}$                       b)  $f_{\alpha} - f_{\beta}$                       c)  $f_T = h_{fe} f_{\beta}$                       d)  $f_T = h_{fb} f_{\alpha}$

28.  $f_T$  in terms of  $f_{\beta}$  is given by \_\_\_\_\_.

- a)  $f_T = h_{fe} f_{\alpha}$                       b)  $f_{\alpha} - f_{\beta}$                       c)  $f_T = h_{fe} f_{\beta}$                       d)  $f_T = h_{fb} f_{\alpha}$

29. Formula for gain in dB in terms of power levels  $P_1$ ,  $P_2$  is \_\_\_\_\_.

- a)  $10 \log (P_2/P_1)$       b)  $20 \log (P_2/P_1)$       c)  $\log (P_2/P_1)$       d)  $1/2 \log (P_2/P_1)$

30. Formula for gain in dB in terms of voltage levels  $V_1$ ,  $V_2$  is \_\_\_\_\_.

- a)  $10 \log (V_2/V_1)$       b)  $20 \log (V_2/V_1)$       c)  $\log (V_2/V_1)$       d)  $1/2 \log (V_2/V_1)$

31. Formula for gain in dB in terms of current levels  $I_1$ ,  $I_2$  is \_\_\_\_\_.

- a)  $10 \log (I_2/I_1)$       b)  $20 \log (I_2/I_1)$       c)  $\log (I_2/I_1)$       d)  $1/2 \log (I_2/I_1)$

32. At  $f=f_T$ ,  $|A_i| =$

- a) 0                      b)  $\frac{1}{2}$                       c) 1                      d)  $\frac{1}{\sqrt{2}}$

33. Formula for gain in bel in terms of power levels  $P_1, P_2$  is \_\_\_\_\_.

- a)  $10 \log (P_2/P_1)$       b)  $20 \log (P_2/P_1)$       c)  $\log (P_2/P_1)$       d)  $\frac{1}{2} \log (P_2/P_1)$

34. At very high frequencies, reactance of capacitor is almost \_\_\_\_\_

- a) 0                      b) 1                      c)  $\infty$                       d) independent of ' $f$ '

35. At very low frequencies, reactance of capacitor is almost \_\_\_\_\_

- a) 0                      b) 1                      c)  $\infty$                       d) independent of ' $f$ '

36. The cut off frequency at which CB short circuit forward current transfer ratio drops to 3dB from its value at low frequencies is called \_\_\_\_\_

- a)  $f_T$                       b)  $f_\gamma$                       c)  $f_\beta$                       d)  $f_\alpha$

37. The cut off frequency at which CE short circuit forward current transfer ratio drops to 3dB from its value at low frequencies is called \_\_\_\_\_

- a)  $f_T$                       b)  $f_\gamma$                       c)  $f_\beta$                       d)  $f_\alpha$

38. \_\_\_\_\_ represents maximum attainable bandwidth of CE amplifier.

- a)  $f_T$                       b)  $f_\beta$                       c)  $f_\gamma$                       d)  $f_\alpha$

39. Which of the following relation is correct?

- a)  $f_\beta < f_\alpha$       b)  $f_T < f_\beta$       c)  $f_T > f_\alpha$       d)  $f_\alpha < f_\beta$

40. Relation between  $f_\alpha, f_\beta$  and  $f_T$  is \_\_\_\_\_

- a)  $f_T < f_\beta < f_\alpha$       b)  $f_\beta < f_T < f_\alpha$       c)  $f_T > f_\alpha > f_\beta$       d)  $f_\alpha < f_\beta < f_T$

### UNIT-III

1. The disadvantage single stage amplifier is \_\_\_\_\_.

- a) high gain      b) low gain      c) low bandwidth      d) high bandwidth

2. In multistage amplifier, \_\_\_\_\_ of one stage is connected to \_\_\_\_\_ of next stage.

- a) output, input      b) output, output      c) input, input      d) input, output

3. Advantage of cascading is \_\_\_\_\_.

- a) high gain      b) correct i/p impedance      c) correct o/p impedance      d) all

4. Cascaded amplifier means \_\_\_\_\_ amplifier followed by \_\_\_\_\_ amplifier.

- a) CE, CE      b) CE, CB      c) CE, CC      d) CB, CE

5. Cascode amplifier means \_\_\_\_\_ amplifier followed by \_\_\_\_\_ amplifier.

- a) CC, CE      b) CE, CB      c) CC, CC      d) CB, CB

6. \_\_\_\_\_ Types of coupling schemes are used in amplifiers.

- a) RC      b) TC      c) Direct      d) all

7. Different coupling schemes used in amplifiers are \_\_\_\_\_.

- a) RC      b) TC      c) Direct      d) all

8. Advantages of coupling networks are \_\_\_\_\_ and \_\_\_\_\_.

- a) less gain      b) transfers dc, isolates ac      c) transfers ac, isolates dc      d) less BW

9. Coupling network isolates \_\_\_\_\_ of one stage to the next stage.

- a) ac                      b) dc                      c) dc, ac                      d) ac output

  10. \_\_\_\_\_ coupling is most commonly used coupling scheme in multistage amplifiers.  
a) RC                      b) TC                      c) Direct                      d) RLC
  11. \_\_\_\_\_ coupling scheme is least expensive.  
a) RC                      b) TC                      c) Direct                      d) RLC
  12. \_\_\_\_\_ coupling scheme has satisfactory frequency response.  
a) RC                      b) TC                      c) Direct                      d) RLC
  13. In \_\_\_\_\_ coupling, signal developed across  $R_C$  is coupled through  $C'$  into base of next stage.  
a) RC                      b) TC                      c) Direct                      d) RLC
  14. Amplifier which uses Resistance capacitance coupling scheme are called as \_\_\_\_\_ amplifiers.  
a) RC                      b) TC                      c) Direct                      d) RLC
  15. In \_\_\_\_\_ coupling, primary winding of transformer acts as a collector load and secondary winding transfers the ac output signal directly to the base of next stage.  
a) RC                      b) TC                      c) Direct                      d) RLC
  16. \_\_\_\_\_ coupling scheme has very high voltage gain.  
a) RC                      b) TC                      c) Direct                      d) RLC
  17. \_\_\_\_\_ coupling scheme has high level of impedance matching.  
a) RC                      b) TC                      c) Direct                      d) RLC
  18. \_\_\_\_\_ coupling scheme was very expensive.  
a) RC                      b) TC                      c) Direct                      d) RLC
  19. Amplifiers which uses transformer coupling scheme are called as \_\_\_\_\_ amplifiers.  
a) RC                      b) TC                      c) Direct                      d) RLC
  20. In \_\_\_\_\_ coupling, ac output signal is fed directly to the next stage.  
a) RC                      b) TC                      c) Direct                      d) RLC
  21. In \_\_\_\_\_ coupling, no reactive elements are used.  
a) RC                      b) TC                      c) Direct                      d) RLC
  22. In \_\_\_\_\_ coupling, special dc voltage level circuits are used.  
a) RC                      b) TC                      c) Direct                      d) RLC
  23. Amplifiers which uses direct coupling scheme are called as \_\_\_\_\_ amplifiers.  
a) RC                      b) Direct                      c) TC                      d) RLC
  24. Entire frequency range is divided into \_\_\_\_\_ ranges.  
a) 1                      b) 2                      c) 3                      d) 4
  25. One advantage of RC coupling is \_\_\_\_\_.  
a) cheap                      b) good response                      c) impedance matching                      d) none
  26. \_\_\_\_\_ Coupling gives uniform voltage amplification.  
a) RC                      b) TC                      c) Direct                      d) RLC

27. \_\_\_\_\_ Coupling has minimum possible distortion.  
 a) RC                      b) TC                      c) Direct                      d) RLC
28. Cascode amplifier has voltage gain as that of \_\_\_\_\_ amplifier.  
 a) CE                      b) CB                      c) CC                      d) CE or CB
29. Cascode amplifier has current gain as that of \_\_\_\_\_ amplifier.  
 a) CE                      b) CB                      c) CC                      d) CE or CB
30. Cascode amplifier has input impedance as that of \_\_\_\_\_ amplifier.  
 a) CE or CB                      b) CB                      c) CC                      d) CE
31. Darlington pair transistor is also called as \_\_\_\_\_ transistor,  
 a) power                      b) triple                      c) megabeta                      d) superbeta
32. Main feature of Darlington pair is high \_\_\_\_\_.  
 a) voltage gain    b) current gain                      c) power gain                      d) BW
33. If  $\beta_1$ ,  $\beta_2$  are current gains of two different transistors, then current gain of Darlington pair is given by formula \_\_\_\_\_.  
 a)  $\beta_1 \cdot \beta_2$                       b)  $\beta_1 + \beta_2$                       c)  $2 \cdot \beta_1 \cdot \beta_2$                       d)  $\beta_1 + 2\beta_2$
34. Darlington pair is commonly used in \_\_\_\_\_ amplifier circuits.  
 a) CE & CB                      b) CE                      c) CC                      d) CB
35. Darlington pair amplifier has \_\_\_\_\_ impedance.  
 a) low input                      b) high input                      c) high output                      d) medium input
36. DC input voltage required to bring back output to its original value is \_\_\_\_\_ voltage  
 a) offset                      b) difference                      c) bias                      d) cutoff
37. For two stage amplifiers, upper cutoff frequency is almost \_\_\_\_\_ % of value obtained in single stage.  
 a) 51                      b) 64                      c) 43                      d) 39
38. For two stage amplifiers, lower cutoff frequency is almost \_\_\_\_\_ % of value obtained in single stage.  
 a) 1.96                      b) 1.76                      c) 1.36                      d) 1.56
39. For three stage amplifiers, upper cutoff frequency is almost \_\_\_\_\_ % of value obtained in single stage.  
 a) 39                      b) 64                      c) 43                      d) 51
40. For three stage amplifiers, lower cutoff frequency is almost \_\_\_\_\_ % of value obtained in single stage.  
 a) 1.76                      b) 1.36                      c) 1.96                      d) 1.56

#### **UNIT-IV**

1. Other name of large signal amplifier is \_\_\_\_\_.  
 a) voltage                      b) current                      c) power                      d) super voltage
2. Based on BJT operation, power amplifiers are classified as \_\_\_\_\_.  
 a) class-A, AB                      b) class-B                      c) class-C                      d) all
3. In a Class-A amplifier, output transistor conducts for \_\_\_\_\_.  
 a)  $\theta = 180^\circ$                       b)  $\theta = 90^\circ$                       c)  $\theta = 270^\circ$                       d)  $\theta = 0^\circ$
4. Theoretical max. Efficiency in a Class-A amplifier is \_\_\_\_\_.

- a) 25                      b) 50                      c) 78.5                      d) 100
5. Theoretical max. Efficiency for a series fed Class-A amplifier is \_\_\_\_\_.
- a) 50                      b) 25                      c) 78.5                      d) 100
6. Theoretical max. Efficiency in a Class-A amplifier by using inductors or transformers is \_\_\_\_\_.
- a) 25                      b) 78.5                      c) 50                      d) 100
7. In Class-B amplifier, transistors conduct for \_\_\_\_\_.
- a)  $\theta = 180^\circ$                       b)  $\theta = 90^\circ$                       c)  $\theta = 270^\circ$                       d)  $\theta = 360^\circ$
8. Theoretical max. Efficiency in Class-B amplifier is \_\_\_\_\_.
- a) 25                      b) 50                      c) 78.5                      d) 100
9. Class-A amplifier means BJT conduction takes place for \_\_\_\_\_.
- a) half cycle                      b) full cycle                      c)  $\frac{1}{4}$  full cycle                      d)  $\frac{3}{4}$  full cycle
10. Class-B amplifier means BJT conduction takes place for \_\_\_\_\_.
- a) half cycle                      b) full cycle                      c)  $\frac{1}{4}$  full cycle                      d)  $\frac{3}{4}$  full cycle
11. Class-AB amplifier means BJT conduction takes place for \_\_\_\_\_.
- a) half cycle                      b) full cycle                      c)  $\frac{1}{4}$  full cycle                      d)  $\frac{3}{4}$  full cycle
12. Class-C amplifier means BJT conduction takes place for \_\_\_\_\_.
- a) half cycle                      b) full cycle                      c)  $\frac{1}{4}$  full cycle                      d)  $\frac{3}{4}$  full cycle
13. Formula for efficiency is given by \_\_\_\_\_.
- a)  $P_{ac} / P_{dc}$                       b)  $1 + P_{ac} / P_{dc}$                       c)  $P_{ac} + P_{dc}$                       d)  $1 - P_{ac} / P_{dc}$
14. Amplitude distortion is also called as \_\_\_\_\_ distortion.
- a) Non-Linear                      b) phase                      c) frequency                      d) all
15. The second harmonic distortion in percentage is given by \_\_\_\_\_ \* 100.
- a)  $B_3/B_1$                       b)  $B_2/B_1$                       c)  $B_1/B_2$                       d)  $B_1/B_4$
16. Total Harmonic Distortion is denoted by \_\_\_\_\_.
- a) P                      b) w                      c) t                      d) D
17. Effective resistance formula for transformer coupled amplifier is given by \_\_\_\_\_.
- a)  $R_L/n^2$                       b)  $R_L \cdot n^2$                       c)  $n^2 / R_L$                       d) none
18. Voltage transformation ratio 'n' is given by \_\_\_\_\_.
- a)  $N_1/N_2$                       b)  $N_1+N_2$                       c)  $N_1-N_2$                       d)  $N_2/N_1$
19. Class-B amplifiers have \_\_\_\_\_ output power than Class-A amplifier.
- a) less                      b) high                      c) zero                      d) unity
20. Class-B amplifiers have \_\_\_\_\_ efficiency than Class-A amplifier.
- a) high                      b) less                      c) zero                      d) unity
21. Thermal resistance is denoted by \_\_\_\_\_.
- a) TR                      b)  $\Theta$                       c)  $\theta$                       d)  $R'$
22. Thermal resistance is measured in \_\_\_\_\_.
- a)  $\Omega$                       b)  $\theta$                       c)  $^\circ\text{C/W}$                       d)  $\text{W/C}$



23. Thermal resistance formula is given by \_\_\_\_\_.  
 a)  $\Delta T/P$                       b)  $\Delta P/T$                       c)  $T.P$                       d)  $R.T$
24. Junction Temperatures of transistor can be reduced by using \_\_\_\_\_.  
 a) neutralization                      b) heat sink                      c) biasing                      d) both a,b
25. Different types of heat sinks are \_\_\_\_\_.  
 a) fin                      b) metal sheet                      c) washer                      d) all
26. Heat sinks are used to \_\_\_\_\_.  
 a) reduce heat                      b) increase R value                      c) avoid oscillations                      d) decrease C value
27. Different types of low power transistor heat sinks are \_\_\_\_\_.  
 a) fin                      b) metal sheet                      c) washer                      d) both fin, washer
28. Change in shape of output wave w.r.t input wave is called as \_\_\_\_\_.  
 a) biasing                      b) neutralization                      c) distortion                      d) stabilization
29. Cross over distortion is observed in \_\_\_\_\_ amplifiers.  
 a) class-A                      b) class-C                      c) class-D                      d) class-B
30. \_\_\_\_\_ is ratio of rms value of all harmonics to rms value of fundamental.  
 a) B2                      b) THD                      c) B1                      d) P
31. \_\_\_\_\_ is the range of  $\beta$  for power transistor.  
 a) low                      b) medium                      c) high                      d) very high
32. h-parameter model is not applicable to \_\_\_\_\_ amplifier.  
 a) voltage                      b) current                      c) power                      d) CE
33. \_\_\_\_\_ is one of the switching amplifiers.  
 a) class-A                      b) class-C                      c) class-D                      d) class-B
34. \_\_\_\_\_ is one of the most efficient power amplifiers.  
 a) class-A                      b) class-AB                      c) class-B                      d) class-D
35. Low power heat dissipation is observed in \_\_\_\_\_ power amplifiers.  
 a) class-A                      b) class-AB                      c) class-B                      d) class-D
36. \_\_\_\_\_ power amplifier is having same type of BJTs.  
 a) class-A                      b) class-AB                      c) class-B push pull                      d) class-B complimentary symmetry push pull
37. \_\_\_\_\_ power amplifier is having opposite type of BJTs.  
 a) class-A                      b) class-AB                      c) class-B push pull                      d) class-B complimentary symmetry push pull
38. The third harmonic distortion is given by \_\_\_\_\_.  
 a)  $B3/B1$                       b)  $B2/B1$                       c)  $B1/B2$                       d)  $B1/B4$
39. The fourth harmonic distortion is given by \_\_\_\_\_.  
 a)  $B3/B1$                       b)  $B2/B1$                       c)  $B4/B1$                       d)  $B1/B4$
40. THD is also called as \_\_\_\_\_ factor  
 a) Quality                      b) Distortion                      c) Quiescent                      d) Difference

#### UNIT-V

1. Tuned circuit means parallel arrangement of \_\_\_\_\_.  
 a) R,C                      b) L,C                      c) R,L                      d) L, C, R
2. Advantage of tuned amplifier is \_\_\_\_\_.  
 a) narrow BW      b) wider BW                      c) low gain                      d) high gain
3. Formula for resonant frequency  $f_0$  is given by \_\_\_\_\_.  
 a)  $1/(2\pi\sqrt{LC})$       b)  $\pi\sqrt{LC}$                       c)  $1/(2\pi\sqrt{RC})$                       d)  $1/(\pi\sqrt{LC})$
4. Response of tuned amplifier is \_\_\_\_\_ at resonant frequency and for frequencies below  $f_0$  and above  $f_0$ , response will \_\_\_\_\_.  
 a) zero, decrease      b) min, increase                      c) max, decrease                      d) unity, increase
5. At resonance, tuned circuit act as \_\_\_\_\_.  
 a) capacitive                      b) inductive                      c) resistive                      d) neutral
6. At resonance, both Voltage and Current are \_\_\_\_\_.  
 a) in phase                      b) out of phase                      c) V lags I                      d) V leads I
7. For frequencies above  $f_0$ , tuned circuit act as \_\_\_\_\_.  
 a) resistive                      b) inductive                      c) neutral                      d) capacitive
8. For frequencies above  $f_0$ , Current \_\_\_\_\_ applied Voltage.  
 a) in phase                      b) has no relation                      c) lags                      d) leads
9. For frequencies below  $f_0$ , tuned circuit act as \_\_\_\_\_.  
 a) resistive                      b) inductive                      c) capacitive                      d) neutral
10. For frequencies below  $f_0$ , Current \_\_\_\_\_ applied Voltage.  
 a) in phase                      b) has no relation                      c) lags                      d) leads
11. Gain of transistor amplifier is \_\_\_\_\_ proportional to its load impedance.  
 a) directly                      b) inversely                      c) no effect                      d) negligible
12. A parallel tuned circuit has \_\_\_\_\_ impedance at its resonant frequency.  
 a) zero                      b) low                      c) high                      d) unity
13. Tuned amplifiers are used for amplification of \_\_\_\_\_ of frequencies.  
 a) narrow band      b) wider band                      c) KHz                      d) MHz
14. Tuned amplifiers are classified into \_\_\_\_\_ no. of types.  
 a) 1                      b) 2                      c) 3                      d) 4
15. Small signal Tuned amplifiers are operated under Class \_\_\_\_\_ mode as power involved is \_\_\_\_\_.  
 a) C, less                      b) B, min                      c) AB, max                      d) A, less
16. Small signal Tuned amplifiers has \_\_\_\_\_ distortion.  
 a) zero                      b) min.                      c) max.                      d) medium
17. Large signal Tuned amplifiers are operated under Class \_\_\_\_\_ mode as power involved is \_\_\_\_\_.  
 a) C, less                      b) B, min                      c) AB, max                      d) A, less
18. Large signal Tuned amplifiers has \_\_\_\_\_ efficiency.  
 a) little                      b) min.                      c) max.                      d) medium

19. Q-factor means \_\_\_\_\_.  
 a) operating      b) Quiescent      c) power      d) Quality
20. Relation between Q-factor and BW is \_\_\_\_\_.  
 a)  $Q=f_0/BW$       b)  $f_0=Q.BW$       c)  $f_0=Q/BW$       d)  $f_0/BW=Q$
21. For high values of Q, BW is \_\_\_\_\_.  
 a) zero      b) min.      c) max.      d) medium
22. For low values of Q, BW is \_\_\_\_\_.  
 a) zero      b) min.      c) max.      d) medium
23. No. of tuned amplifier stages are cascaded to \_\_\_\_\_.  
 a) decrease  $V_0$       b) increase  $V_0$       c) decrease  $V_i$       d) decrease  $V_i$
24. Single tuned amplifier uses \_\_\_\_\_ parallel resonant circuit per each stage.  
 a) 0      b) 2      c) 1      d) 3
25. Double tuned amplifier uses \_\_\_\_\_ parallel resonant circuits per each stage.  
 a) 0      b) 2      c) 1      d) 3
26. Single tuned amplifier uses \_\_\_\_\_ coupling.  
 a) L      b) C      c) TC      d) all
27. Double tuned amplifier uses \_\_\_\_\_ coupling.  
 a) R      b) C      c) TC      d) all
28. Stagger tuned amplifier uses no. of \_\_\_\_\_ tuned amplifiers in cascade.  
 a) single      b) double      c) both a,b      d) none
29. In Single tuned amplifiers cascading, all tuned circuits are tuned to \_\_\_\_\_ frequency.  
 a) different      b) same      c) twice      d) thrice
30. For tuned amplifiers,  $\delta$  means \_\_\_\_\_ variation.  
 a) fractional frequency      b) fractional BW      c) frequency      d) BW
31. For tuned amplifiers, formula for  $\delta$  is given by \_\_\_\_\_.  
 a)  $(f-f_0)/f$       b)  $(f_0-f)/f$       c)  $(f+f_0)/f$       d)  $(f_1-f_0)/f$
32. For double tuned amplifiers, factor 'b' means \_\_\_\_\_.  
 a) constant of BJT      b) error      c) distortion      d) coeff. of coupling
33. Range of factor 'b' is from \_\_\_\_\_ and \_\_\_\_\_.  
 a) 0, 1      b) 1, 1.7      c) 0, 1.7      d) 1, 2.7
34. For double tuned amplifiers, factor 'b' is always \_\_\_\_\_.  
 a) more than 1      b) less than 1      c) 0      d) 1
35. Neutralization is to \_\_\_\_\_ in tuned amplifiers.  
 a) avoid distortion      b) increase gain      c) avoid oscillations      d) reduce heat
36. Q-factor of inductor is \_\_\_\_\_.  
 a)  $\omega L/R$       b)  $\omega R/L$       c)  $L/\omega R$       d)  $\omega/LR$
37. Q-factor of capacitor is \_\_\_\_\_.

- a)  $\omega R/C$       b)  $\omega C/R$       c)  $1/\omega CR$       d)  $\omega/RC$

38. Q-factor of lossy capacitor is \_\_\_\_\_.

- a)  $\omega R_p/C$       b)  $\omega C/R_p$       c)  $1/\omega CR_p$       d)  $\omega C R_p$

39. In Hazeltine Neutralization technique  $C_N$  is connected from bottom of coil to \_\_\_\_ of transistor.

- a) emitter      b) base      c) collector      d) both base and collector

40. In modified Hazeltine Neutralization technique  $C_N$  is connected from base of transistor and \_\_\_\_.

- a) collector      b) emitter      c) ground      d) lower end of next stage

**KEY:**

**UNIT-1:**

1. A	2.C	3.B	4.A	5.B	6.A	7.B	8.D	9.C	10.A
11.D	12.A	13.B	14.D	15.C	16.C	17.B	18.C	19.D	20.A
21.A	22.C	23.B	24.C	25.A	26.D	27.A	28.B	29.D	30.D
31.B	32.A	33.C	34.B	35.D	36.C	37.D	38.C	39.A	40.C

**UNIT-2:**

1.B	2.D	3.A	4.B	5.D	6.D	7.C	8.C	9.C	10.B
11.D	12.A	13.B	14.C	15.B	16.D	17.C	18.A	19.D	20.A
21.C	22.A	23.C	24.D	25.B	26.A	27.D	28.C	29.A	30.B
31.B	32.C	33.C	34.A	35.C	36.D	37.C	38.B	39.A	40.B

**UNIT-3:**

1.B	2.A	3.D	4.A	5.B	6.D	7.D	8.C	9.B	10.A
11.C	12.A	13.A	14.A	15.B	16.B	17.B	18.B	19.B	20.C
21.C	22.C	23.B	24.C	25.A	26.A	27.A	28.B	29.A	30.D
31.D	32.B	33.A	34.C	35.B	36.A	37.B	38.D	39.D	40.C

**UNIT-4:**

1.C	2.D	3.D	4.A	5.B	6.C	7.A	8.C	9.B	10.A
11.D	12.C	13.A	14.A	15.B	16.D	17.A	18.D	19.B	20.A
21.B	22.C	23.A	24.B	25.D	26.A	27.D	28.C	29.D	30.B
31.A	32.C	33.C	34.D	35.D	36.C	37.D	38.A	39.C	40.B

**UNIT-5:**

1.B	2.A	3.A	4.C	5.C	6.A	7.D	8.D	9.B	10.C
11.A	12.C	13.A	14.B	15.D	16.B	17.C	18.C	19.D	20.A
21.B	22.C	23.B	24.C	25.B	26.D	27.C	28.A	29.B	30.A

31.A

32.D

33.B

34.A

35.C

36.A

37.C

38.D

39.B

40.D