

## Electronic Circuit Analysis (ECA) Mid-1 Questions

### Long Answer Questions

1. Explain in detail about voltage series feedback amplifier with necessary circuits. Derive i)  $A_F$  ii)  $Z_{if}$  iii)  $Z_{of}$
2. Explain in detail about voltage shunt feedback amplifier with necessary circuits.. Derive i)  $A_F$  ii)  $Z_{if}$  iii)  $Z_{of}$
3. Explain in detail about current series feedback amplifier with necessary circuits. Derive i)  $A_F$  ii)  $Z_{if}$  iii)  $Z_{of}$
4. Explain in detail about current shunt feedback amplifier with necessary circuits. Derive i)  $A_F$  ii)  $Z_{if}$  iii)  $Z_{of}$
5. Define feedback. Draw the block diagram of general feedback amplifier and explain in detail. Classify different types of it.
6. Write the characteristics of negative feedback amplifiers. Give a comparison between different types of feedback amplifiers.
7. Define oscillator. Classify different types of it. Draw the general block diagram of oscillator and explain in detail. Write the conditions for oscillations.
8. Give a comparison between different types of oscillators.
9. What are the advantages, disadvantages and applications of different oscillators?
10. Explain the generalized analysis of LC oscillators with equations.
11. Explain about Colpitts oscillator with the help of circuit and Derive equation for frequency of oscillations.
12. Explain about Hartley oscillator with the help of circuit and Derive equation for frequency of oscillations.
13. Explain about Wien Bridge oscillator with the help of circuit and Derive equation for frequency of oscillations.
14. Explain about RC phase shift oscillator with the help of circuit and Derive equation for frequency of oscillations.
15. Write in detail about Crystal oscillator with necessary circuits and equations.
16. Write in detail about stability of oscillators.
17. Draw the circuit of Giaccolletto model of BJT in CE mode and explain its features.
18. Write the relationship between low frequency h-parameters and high frequency parameters.
19. Define  $f_L$ ,  $f_H$ ,  $f_T$ ,  $f_{\alpha}$ ,  $f_{\beta}$ , BW, feedback, oscillator, piezoelectric effect, frequency stability.
20. **All types of problems and definitions are important.**

\*\*\*\*\*

**Note:** Unit-1 carries 30Marks, Unit-2 carries 20Marks (upto topics covered)

### **Electronic Circuit Analysis (ECA) Mid-1 bits**

1. The gain of an amplifier with Negative feedback is given by \_\_\_\_\_.
2. The disadvantage of negative feedback is that gain \_\_\_\_\_.
3. With series feedback, input resistance of an amplifier will \_\_\_\_\_.
4. If negative feedback is used in amplifiers then Noise will \_\_\_\_\_.
5. If negative feedback is used in amplifiers then Bandwidth will \_\_\_\_\_.
6. If negative feedback is used in amplifiers then lower cut-off frequency will \_\_\_\_\_.
7. If negative feedback is used in amplifiers then higher cut-off frequency will \_\_\_\_\_.
8. If negative feedback is used in amplifiers then gain will \_\_\_\_\_.
9. If negative feedback is used in amplifiers then distortion will \_\_\_\_\_.
10. With shunt feedback, input resistance of an amplifier will \_\_\_\_\_.
11. Voltage series feedback amplifier is also called as \_\_\_\_\_.
12. Voltage shunt feedback amplifier is also called as \_\_\_\_\_.
13. Current series feedback amplifier is also called as \_\_\_\_\_.
14. Current shunt feedback amplifier is also called as \_\_\_\_\_.
15. Oscillator is a circuit which converts \_\_\_\_\_ to \_\_\_\_\_.
16. Sinusoidal oscillators are also called as \_\_\_\_\_.
17. Non-Sinusoidal oscillators are also called as \_\_\_\_\_.
18. Classification of oscillators based on output waveform are divided into \_\_\_\_\_ and \_\_\_\_\_.
19. Examples of Sinusoidal oscillators are \_\_\_\_\_.
20. Classification of oscillators based on working are divided into \_\_\_\_\_ and \_\_\_\_\_.
21. Classification of oscillators based on type of circuit are divided into \_\_\_\_\_ and \_\_\_\_\_.
22. Examples of non-sinusoidal waveforms are \_\_\_\_\_.
23. An oscillator uses \_\_\_\_\_ type of feedback.
24. RF oscillators are also called as \_\_\_\_\_.
25. AF oscillator has \_\_\_\_\_ range of frequencies.
26. RF oscillator has \_\_\_\_\_ range of frequencies.
27. VHF oscillator has \_\_\_\_\_ range of frequencies.
28. UHF oscillator has \_\_\_\_\_ range of frequencies.
29. MWF oscillator has \_\_\_\_\_ range of frequencies.
30. If  $a = bx$ , then  $x =$  \_\_\_\_\_.
31.  $\log_{10} =$  \_\_\_\_\_ and  $\log_{10} n =$  \_\_\_\_\_.
32. Logarithm taken to the base 'e' is called as \_\_\_\_\_.
33. Logarithm taken to the base '10' is called as \_\_\_\_\_.

34. Hybrid-pi parameters are \_\_\_\_\_.
35. Examples of LC oscillators are \_\_\_\_\_ circuits.
36. Examples of RC oscillators are \_\_\_\_\_ circuits.
37. \_\_\_\_\_ Oscillator exhibits piezoelectric effect.
38. Necessary conditions to be satisfied by any oscillator circuit are called as \_\_\_\_\_.
39. Two conditions to be satisfied by any oscillator circuit are given by \_\_\_\_\_ and \_\_\_\_\_.
40. Advantage of RC oscillator is \_\_\_\_\_.
41. Disadvantage of RC oscillator is \_\_\_\_\_.
42. RC phase shift oscillator has \_\_\_\_\_ no. of identical RC sections.
43. Each RC section in RC phase shift oscillator generates \_\_\_\_\_ amount of phase shift.
44. Advantage of LC oscillator is \_\_\_\_\_.
45. Disadvantage of LC oscillator is \_\_\_\_\_.
46. In Hartley Oscillator \_\_\_\_\_ are variable and \_\_\_\_\_ is constant.
47. In Colpitts Oscillator \_\_\_\_\_ are variable and \_\_\_\_\_ is constant.
48. In Wienbridge oscillator circuit, feedback network generates \_\_\_\_\_ amount of phase shift.
49. In tuned oscillator circuit, when supply is switched ON \_\_\_\_\_ is produced in tank circuit.
50. Other name of LC oscillators are \_\_\_\_\_.
51. Frequency stability of Crystal oscillator is in the range of \_\_\_\_\_.
52. Crystal oscillator can be used to generate frequencies of range \_\_\_\_\_.
53. Types of crystals are \_\_\_\_\_ and \_\_\_\_\_.
54. Examples of Piezo-electric materials are \_\_\_\_\_.
55. Hybrid-pi model is also called as \_\_\_\_\_.
56. \_\_\_\_\_ Capacitors effect is considered in low frequency response of amplifier circuit.
57. \_\_\_\_\_ Capacitors effect is considered in high frequency response of amplifier circuit.
58. Range of  $r_{bb'}$  is \_\_\_\_\_.
59. Range of  $r_{b'c}$  is \_\_\_\_\_.
60. Range of  $r_{b'e}$  is \_\_\_\_\_.
61. Range of  $r_{ce}$  is \_\_\_\_\_.
62. Range of  $C_{b'c}$  is \_\_\_\_\_.
63. Range of  $C_{b'e}$  is \_\_\_\_\_.
64. Formula of  $r_{bb'}$  is \_\_\_\_\_.
65. Formula of  $r_{b'c}$  is \_\_\_\_\_.
66. Formula of  $r_{b'e}$  is \_\_\_\_\_.
67. Formula of  $C_{b'c}$  is \_\_\_\_\_.
68. Formula of  $C_{b'e}$  is \_\_\_\_\_.

69. Formula of  $g_m$  is \_\_\_\_\_.
70. Formula of  $V_T$  in terms of  $T$  in  $^{\circ}C$  is \_\_\_\_\_.
71. Formula of  $h_{ie}$  in terms of  $r_{bb'}$  is \_\_\_\_\_.
72. Formula of Bandwidth is \_\_\_\_\_.
73. Relation between dB and Bel is \_\_\_\_\_.
74.  $f_T$  is called as \_\_\_\_\_.
75.  $f_{\beta}$  is called as \_\_\_\_\_.
76.  $f_{\alpha}$  is called as \_\_\_\_\_.
77.  $f_{\beta}$  is also indicated as \_\_\_\_\_.
78.  $f_{\alpha}$  is also indicated as \_\_\_\_\_.
79.  $f_T$  in terms of  $f_{\alpha}$  is given by \_\_\_\_\_.
80.  $f_T$  in terms of  $f_{\beta}$  is given by \_\_\_\_\_.
81. The frequency of oscillations for Colpitt's oscillator is  $f_0 =$  \_\_\_\_\_.
82. The frequency of oscillations for Hartley oscillator is  $f_0 =$  \_\_\_\_\_.
83. The frequency of oscillations for RC phase shift oscillator is  $f_0 =$  \_\_\_\_\_.
84. The frequency of oscillations for Wienbridge oscillator is  $f_0 =$  \_\_\_\_\_.
85. The frequency of oscillations for Crystal oscillator is \_\_\_\_\_.
86. Advantages of Crystal oscillator are \_\_\_\_\_.
87. Generalized equation of LC oscillators is given by \_\_\_\_\_.
88. The frequency stability of oscillators is depending on \_\_\_\_\_.
89. Frequency stability may be in between \_\_\_\_\_ and \_\_\_\_\_.
90. Frequency may vary because of \_\_\_\_\_.
91. For any oscillator, Variation of frequency with temperature is given by \_\_\_\_\_.
92. Unit for  $S_{w,T}$  are \_\_\_\_\_.
93. Frequency stability is given by formula \_\_\_\_\_.
94. Frequency stability can be increased by \_\_\_\_\_.
95. Range of  $h_{ie}$  is \_\_\_\_\_ and  $h_{oe}$  is \_\_\_\_\_.
96. Range of  $h_{fe}$  is \_\_\_\_\_ and  $h_{re}$  is \_\_\_\_\_.
97. Formula for gain in dB in terms of power levels  $P_1, P_2$  is \_\_\_\_\_.
98. Formula for gain in dB in terms of voltage levels  $V_1, V_2$  is \_\_\_\_\_.
99. Formula for gain in dB in terms of current levels  $I_1, I_2$  is \_\_\_\_\_.
100. **All definitions are important.**

\*\*\*\*\*

## Electronic Circuit Analysis (ECA) Mid-2 Questions

### Long Answer Questions

1. Define amplifier. Classify different types of amplifiers.
2. Explain about different methods of coupling.
3. Explain in detail about RC coupling with necessary circuit. Mention its advantages and disadvantages.
4. Explain in detail about transformer coupling with necessary circuit, advantages and disadvantages.
5. Explain in detail about direct coupling with necessary circuit, advantages and disadvantages.
6. Explain in detail about RC coupling with necessary circuit.
7. Explain different types of coupling. When two identical stages are cascaded, obtain voltage gain, current gain and power gain.
8. Compare different methods of coupling.
9. Derive an equation for voltage gain, current gain, input impedance and output impedance of Darlington emitter follower.
10. Write in detail about Cascode amplifier.
11. Compare Darlington pair and Cascode amplifiers.
12. Define Differential amplifier. Classify different types of it. Compare them.
13. Explain in detail about DC analysis of Differential amplifier using BJT. Derive its factors.
14. Explain in detail about AC analysis of Differential amplifier using BJT. Derive its factors.
15. Compare all Differential amplifiers.
16. Define Power amplifier. Classify different types of it.
17. Describe class-A large signal amplifier and also obtain the efficiency.
18. Define second harmonic distortion. Derive an expression for second harmonic component of transmitter amplifier.
19. Write in detail about Higher order harmonic Distortion with necessary equations.
20. Explain in detail about Class-B Amplifier, derive the efficiency.
21. Draw and explain about Complementary Symmetry push pull amplifier.
22. Draw and explain class-B push pull amplifier.
23. Compare Class-A and Class-B Amplifiers.
24. Compare various types of Power Amplifiers.
25. Define Thermal stability and explain about it in detail.
26. Define Heat sink. Classify different types of it. Write about importance of heat sink in power amplifier.
27. Define Tuned Amplifier. Classify different types of it.
28. Define Q-factor. What are the advantages of tuned amplifiers?
29. Define Q-factor for inductor and derive the Q-factor formula.
30. Define Q-factor for capacitor and derive the Q-factor formula.
31. Define Q-factor for lossy capacitor and derive the Q-factor formula.
32. Define loaded Q and unloaded Q with formulas.

33. Describe the operation of single tuned amplifier with neat circuit diagram and relevant expression.
34. With neat circuit diagram, describe the operation of capacitance single tuned amplifier.
35. Derive the expression for bandwidth and Q factor of single tuned capacitive coupled amplifier.
36. Illustrate the operation of double tuned amplifier with neat circuit diagram and necessary equation.
37. Differentiate Single tuned and double tuned amplifiers.
38. Explain the effect of Cascading Single tuned amplifiers on Band width.
39. Explain the effect of Cascading Double tuned amplifiers on Band width.
40. Write in detail about Staggered tuned amplifiers with its equations and advantages..
41. Explain about the Stability of tuned amplifiers with necessary circuits.
42. Write in detail about Neutralization techniques.
- 43. All definitions and problems are important.**

\*\*\*\*\*

### **Electronic Circuit Analysis (ECA) Mid-2 bits**

1. Multistage amplifier means \_\_\_\_\_.
2. The disadvantage single stage amplifier is \_\_\_\_\_.
3. In multistage amplifier, \_\_\_\_\_ of one stage is connected to \_\_\_\_\_ of next stage.
4. Cascading means \_\_\_\_\_.
5. Advantage of cascading is \_\_\_\_\_.
6. Cascaded amplifier means \_\_\_\_\_.
7. Cascode amplifier means \_\_\_\_\_.
8. \_\_\_\_\_ Types of coupling schemes are used in amplifiers.
9. Different coupling schemes used in amplifiers are \_\_\_\_\_.
10. Advantages of coupling networks are \_\_\_\_\_  
and \_\_\_\_\_.
11. Coupling network transfers \_\_\_\_\_ of one stage to the \_\_\_\_\_ of next stage.
12. Coupling network isolates \_\_\_\_\_ of one stage to the next stage.
13. \_\_\_\_\_ is most commonly used coupling scheme in multistage amplifiers.
14. \_\_\_\_\_ coupling scheme is least expensive.
15. \_\_\_\_\_ coupling scheme has satisfactory frequency response.
16. In \_\_\_\_\_ coupling, signal developed across collector resistor is coupled through capacitor into base of next stage.
17. \_\_\_\_\_ isolates the dc conditions of one stage to next stage.
18. Amplifier which uses Resistance capacitance coupling scheme are called as \_\_\_\_\_ amplifiers.
19. In \_\_\_\_\_ coupling, primary winding of transformer acts as a collector load and secondary winding transfers the ac output signal directly to the base of next stage.

20. \_\_\_\_\_ coupling scheme has very high voltage gain.
21. \_\_\_\_\_ coupling scheme has high level of impedance matching.
22. \_\_\_\_\_ coupling scheme was very expensive.
23. \_\_\_\_\_ coupling scheme is restricted to power amplifiers.
24. Amplifiers which uses transformer coupling scheme are called as \_\_\_\_\_ amplifiers.
25. In \_\_\_\_\_ coupling, ac output signal is fed directly to the next stage.
26. In \_\_\_\_\_ coupling, no reactive elements are used.
27. In \_\_\_\_\_ coupling, special dc voltage level circuits are used.
28. Amplifiers which uses direct coupling scheme are called as \_\_\_\_\_ amplifiers.
29. Direct coupled amplifiers are also called as \_\_\_\_\_.
30. Frequency response means \_\_\_\_\_.
31. Entire frequency range is divided into \_\_\_\_\_ number of ranges.
32. The three frequency ranges are \_\_\_\_\_, \_\_\_\_\_ & \_\_\_\_\_.
33. Lower cutoff frequency means \_\_\_\_\_.
34. Higher cutoff frequency means \_\_\_\_\_.
35. Bandwidth means \_\_\_\_\_.
36. The overall voltage gain of 'n' stages of cascaded amplifier is given by \_\_\_\_\_.
37. The overall phase shift of 'n' stages of cascaded amplifier is given by \_\_\_\_\_.
38. General formula for voltage gain is given by \_\_\_\_\_.
39. General formula for current gain is given by \_\_\_\_\_.
40. General formula for power gain is given by \_\_\_\_\_.
41. One advantage of RC coupling is \_\_\_\_\_.
42. \_\_\_\_\_ Coupling is cheap, small, and light.
43. \_\_\_\_\_ Coupling gives uniform voltage amplification.
44. \_\_\_\_\_ Coupling does not require any coil or transformer.
45. \_\_\_\_\_ Coupling has minimum possible distortion.
46. One disadvantage of RC coupling is \_\_\_\_\_.
47. \_\_\_\_\_ Coupling is noisy in humid weather.
48. \_\_\_\_\_ Coupling has poor impedance matching.
49. Applications of RC coupling are \_\_\_\_\_.
50. Applications of transformer coupled amplifiers are \_\_\_\_\_.
51. Relation between  $N_1$  and  $N_2$  for transformer coupling is given by \_\_\_\_\_.
52. Applications of direct coupling are \_\_\_\_\_.
53. Capacitors are not used in DC amplifiers because \_\_\_\_\_.

54. No. of techniques available for amplifying low frequency signals that change very slowly are \_\_\_\_\_.
55. One technique to amplify low frequency signal is \_\_\_\_\_.
56. Second technique to amplify low frequency signal is \_\_\_\_\_.
57. The drawback of DC amplifiers is \_\_\_\_\_.
58. Voltage offset means \_\_\_\_\_.
59. Offset current means \_\_\_\_\_.
60. Generally Voltage offset is measured in \_\_\_\_\_.
61. Generally offset current is measured in \_\_\_\_\_.
62. Cascode amplifier means \_\_\_\_\_.
63. Drawback of CB amplifier is \_\_\_\_\_.
64. Advantage of CE amplifier is \_\_\_\_\_.
65. Cascode amplifier has voltage gain as that of \_\_\_\_\_ amplifier.
66. Cascode amplifier has current gain as that of \_\_\_\_\_ amplifier.
67. Cascode amplifier has input impedance as that of \_\_\_\_\_ amplifier.
68. Overall voltage gain for cascode amplifier is given by \_\_\_\_\_.
69. Darlington pair transistor is also called as \_\_\_\_\_,
70. Main feature of Darlington pair is \_\_\_\_\_.
71. If  $\beta_1, \beta_2$  are current gains of two different transistors, then current gain of Darlington pair is given by formula \_\_\_\_\_.
72. If two transistors are matched in Darlington pair connection, then current gain of Darlington pair is given by \_\_\_\_\_.
73. Darlington pairs are generally available in \_\_\_\_\_ packages.
74. Darlington pair is commonly used in \_\_\_\_\_ circuit.
75. \_\_\_\_\_ is having high current gain.
76. \_\_\_\_\_ is having high input impedance.
77. Base current of Darlington circuit is given by equation \_\_\_\_\_.
78. Emitter current of Darlington circuit is given by equation \_\_\_\_\_.
79. Emitter voltage of Darlington circuit is given by equation \_\_\_\_\_.
80. Base voltage of Darlington circuit is given by equation \_\_\_\_\_.
81. AC input impedance of Darlington circuit is given by equation \_\_\_\_\_.
82. AC output impedance of Darlington circuit is given by equation \_\_\_\_\_.
83. AC current gain of Darlington circuit is given by equation \_\_\_\_\_.
84. AC voltage gain of Darlington circuit is given by equation \_\_\_\_\_.
85. For 'n' no. of stages, formula for lower cutoff frequency  $f_L$  is given by \_\_\_\_\_.
86. For 'n' no. of stages, formula for higher cutoff frequency  $f_H$  is given by \_\_\_\_\_.
87. For  $n=2$ , upper cutoff frequency changes by \_\_\_\_\_ of value obtained for single stage.
88. For  $n=2$ , lower cutoff frequency changes by \_\_\_\_\_ of value obtained for single stage.



89. For  $n=3$ , upper cutoff frequency changes by \_\_\_\_\_ of value obtained for single stage.
90. For  $n=3$ , lower cutoff frequency changes by \_\_\_\_\_ of value obtained for single stage.
91. Tuned amplifier means \_\_\_\_\_.
92. Tuned circuit means \_\_\_\_\_.
93. Advantage of tuned amplifier is \_\_\_\_\_.
94. Applications of tuned amplifier are \_\_\_\_\_ and \_\_\_\_\_.
95. Formula for resonant frequency  $f_0$  is given by \_\_\_\_\_.
96. Response of tuned amplifier is \_\_\_\_\_ at resonant frequency and for frequencies below  $f_0$  and above  $f_0$ , response will \_\_\_\_\_.
97. At resonance, tuned circuit act as \_\_\_\_\_.
98. At resonance, both Voltage and Current are \_\_\_\_\_.
99. For frequencies above  $f_0$ , tuned circuit act as \_\_\_\_\_.
100. For frequencies above  $f_0$ , Current \_\_\_\_\_ applied Voltage.
101. For frequencies below  $f_0$ , tuned circuit act as \_\_\_\_\_.
102. For frequencies below  $f_0$ , Current \_\_\_\_\_ applied Voltage.
103. Gain of transistor amplifier is \_\_\_\_\_ proportional to its load impedance.
104. A parallel tuned circuit has \_\_\_\_\_ impedance at its resonant frequency.
105. Tuned amplifiers are used for amplification of \_\_\_\_\_ of frequencies.
106. Tuned amplifiers are classified into \_\_\_\_\_ no. of types.
107. Tuned amplifiers are classified as \_\_\_\_\_ and \_\_\_\_\_.
108. Small signal Tuned amplifiers are used for amplification of \_\_\_\_\_ at RF.
109. Small signal Tuned amplifiers are operated under \_\_\_\_\_ mode as power involved is \_\_\_\_\_.
110. Small signal Tuned amplifiers has \_\_\_\_\_ distortion.
111. Small signal Tuned amplifiers has \_\_\_\_\_ efficiency.
112. Large signal Tuned amplifiers are used for amplification of \_\_\_\_\_ at RF.
113. Large signal Tuned amplifiers are operated under \_\_\_\_\_ mode as power involved is \_\_\_\_\_.
113. Large signal Tuned amplifiers has \_\_\_\_\_ distortion.
114. Large signal Tuned amplifiers has \_\_\_\_\_ efficiency.
115. Q-factor means \_\_\_\_\_.
116. Formula for Q-factor \_\_\_\_\_.
117. Q-factor for inductor is given by formula \_\_\_\_\_.
118. Q-factor for capacitor is given by formula \_\_\_\_\_.
119. Q-factor for lossy capacitor is given by formula \_\_\_\_\_.
120. Unloaded Q means \_\_\_\_\_.

121. Loaded Q means \_\_\_\_\_.
122. Formula for Loaded Q is given by \_\_\_\_\_.
123. Relation between Q-factor and BW is \_\_\_\_\_.
124. Q-factor and BW are \_\_\_\_\_ proportional.
125. For high values of Q, BW is \_\_\_\_\_.
126. For low values of Q, BW is \_\_\_\_\_.
127. No. of tuned amplifier stages are cascaded to \_\_\_\_\_.
128. Cascaded tuned amplifiers are classified into \_\_\_\_\_ no. of types.
129. Types of Cascaded tuned amplifier are \_\_\_\_\_.
130. Single tuned amplifier uses \_\_\_\_\_ parallel resonant circuit per each stage.
131. Double tuned amplifier uses \_\_\_\_\_ parallel resonant circuits per each stage.
132. Single tuned amplifier uses \_\_\_\_\_ coupling.
133. Double tuned amplifier uses \_\_\_\_\_ coupling.
134. Stagger tuned amplifier uses no. of \_\_\_\_\_ in cascade.
135. In Single tuned amplifiers cascading, all tuned circuits are tuned to \_\_\_\_\_ frequency.
136. In Double tuned amplifiers cascading, all tuned circuits are tuned to \_\_\_\_\_ frequency.
137. In Double tuned amplifiers all tuned circuits are tuned to \_\_\_\_\_ frequency.
138. Single tuned amplifiers are classified as \_\_\_\_\_ no. of types.
139. Types of Single tuned amplifiers are \_\_\_\_\_.
140. Relative gain formula for single capacitance coupled amplifier is given by \_\_\_\_\_.
141. Phase angle of for single capacitance coupled amplifier is given by \_\_\_\_\_.
142. For tuned amplifiers,  $\delta$  means \_\_\_\_\_.
143. For tuned amplifiers, formula for  $\delta$  is given by \_\_\_\_\_.
144. 3dB BW formula for double tuned amplifier is given by \_\_\_\_\_.
145. For double tuned amplifiers, factor 'b' means \_\_\_\_\_.
146. Range of factor 'b' is from \_\_\_\_\_ and \_\_\_\_\_.
147. For double tuned amplifiers, factor 'b' is always \_\_\_\_\_.
148. Formula for effect of cascading Single tuned amplifiers on BW is \_\_\_\_\_.
149. Formula for effect of cascading Double tuned amplifiers on BW is \_\_\_\_\_.
150. Formula for resultant relative gain for stagger tuned amplifiers is \_\_\_\_\_.
151. Large signal tuned amplifiers are generally operated in \_\_\_\_\_ mode.
152. Conduction angle means \_\_\_\_\_.
153. Neutralization means \_\_\_\_\_.
154. \_\_\_\_\_ Neutralization technique is generally used to avoid oscillations in tuned amplifiers.
155. Other name of large signal amplifier is \_\_\_\_\_.

156. Based on operation, power amplifiers are classified as \_\_\_\_\_.
157. In a Class-A amplifier, output transistor conducts for \_\_\_\_\_.
158. Theoretical max. Efficiency in a Class-A amplifier is \_\_\_\_\_.
159. Theoretical max. Efficiency for a series fed Class-A amplifier is \_\_\_\_\_.
160. Theoretical max. Efficiency in a Class-A amplifier by using inductors or transformers is \_\_\_\_\_.
161. In Class-B amplifier, transistors conduct for \_\_\_\_\_.
162. Theoretical max. Efficiency in Class-B amplifier is \_\_\_\_\_.
163. Class-A amplifier means \_\_\_\_\_.
164. Class-B amplifier means \_\_\_\_\_.
165. Class-AB amplifier means \_\_\_\_\_.
166. Class-C amplifier means \_\_\_\_\_.
167. Formula for efficiency is given by \_\_\_\_\_.
168. Formula for input power of Class-A amplifier is given by \_\_\_\_\_.
169. Formula for output power of Class-A amplifier is given by \_\_\_\_\_.
170. Amplitude distortion is also called as \_\_\_\_\_.
171. Distortion means \_\_\_\_\_.
172. Harmonic Distortion is caused by \_\_\_\_\_.
173. The second harmonic distortion in percentage is given by \_\_\_\_\_.
174. Total Harmonic Distortion means \_\_\_\_\_.
175. Total Harmonic Distortion is also called as \_\_\_\_\_.
176. Total Harmonic Distortion is denoted by \_\_\_\_\_.
177. Total Harmonic Distortion is given by formula \_\_\_\_\_.
178. The max. possible Total Harmonic Distortion for high quality audio amplifiers is \_\_\_\_\_.
179. As the power level increases, the harmonic distortions will be \_\_\_\_\_.
180. Effective resistance formula for transformer coupled amplifier is given by \_\_\_\_\_.
181. Voltage transformation ratio 'n' is given by \_\_\_\_\_.
182. Conduction angle in Class-A amplifiers is \_\_\_\_\_.
183. Conduction angle in Class-B amplifiers is \_\_\_\_\_.
184. Advantages of Class-B amplifiers are \_\_\_\_\_.
185. Class-B amplifiers have \_\_\_\_\_ output power than Class-A amplifier.
186. Class-B amplifiers have \_\_\_\_\_ efficiency than Class-A amplifier.
187. Class-B amplifiers have \_\_\_\_\_ power loss than Class-A amplifier.
188. Class-B amplifiers are having \_\_\_\_\_ type of distortion.
189. Advantage of Class-B push pull amplifier is \_\_\_\_\_.
190. Disadvantage of Class-B push pull amplifier is \_\_\_\_\_.
191. Phase inverter means \_\_\_\_\_.
192. Drawbacks of phase inverters are \_\_\_\_\_.

193. Thermal resistance means \_\_\_\_\_.
194. Thermal resistance is denoted by \_\_\_\_\_.
195. Thermal resistance is measured in \_\_\_\_\_.
196. Thermal resistance min. value is \_\_\_\_\_ and max. value is \_\_\_\_\_.
197. Thermal resistance formula is given by \_\_\_\_\_.
198. Junction Temperatures of transistor can be reduced by using \_\_\_\_\_.
199. Different types of heat sinks are \_\_\_\_\_.
200. Heat sinks are used to \_\_\_\_\_.
201. Different types of low power transistor heat sinks are \_\_\_\_\_.
202. \_\_\_\_\_ and \_\_\_\_\_ types heat sinks are used for high power transistors.

\*\*\*\*\*